 


ORGANIZAÇÃO E ARQUITETURA DE COMPUTADORES

AULA 20

Prof. Max Santana Rolemberg Farias
max.santana@univasf.edu.br
Colegiado de Engenharia de Computação






PROCESSADOR DIDÁTICO

myRISCVv1



PROCESSADOR myRISCVv1

DATAPATH INSTRUCTION DECODER


 


Componente fundamental que desempenha um papel crítico na interpretação das instruções.

- Traduz a representação binária das instruções em sinais de controle significativos e dados.
- Garante que o processador entenda qual operação executar, quais operandos usar e como manipular dados com base no formato de instrução


PROCESSADOR myRISCVv1

DATAPATH INSTRUCTION DECODER

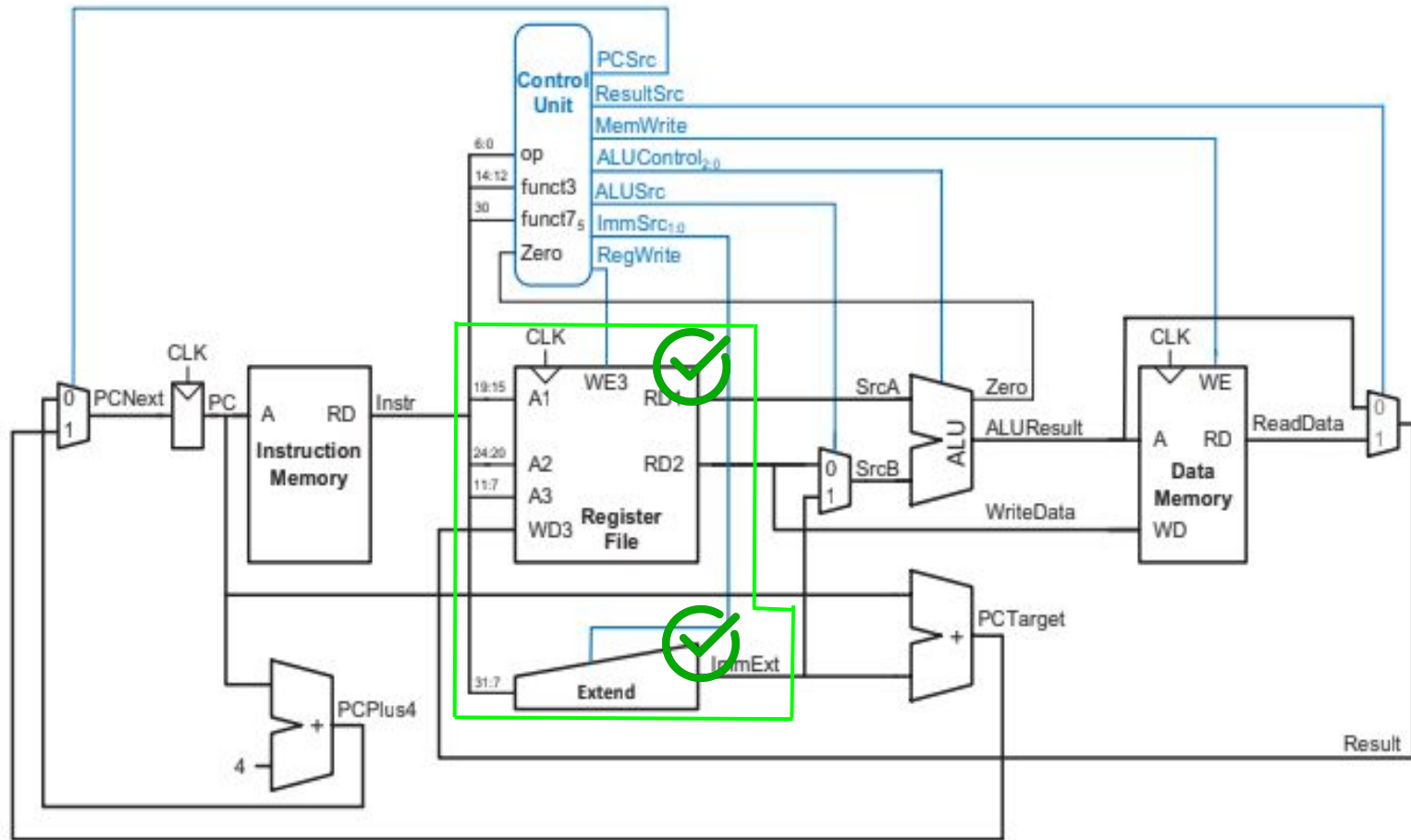 

PROCESSADOR myRISCVv1

DATAPATH IDECODER

 

```
-- Instruction decode
-- myRISCVv1
--
-- Prof. Max Santana (2025)
-- CECComp/Univasf
--
```

```
library ieee;
use ieee.std_logic_1164.all;

entity idecoder is
  port(
    clk    : in std_logic;
    rst    : in std_logic;
    instr  : in std_logic_vector(31 downto 0);
    we     : in std_logic;
    immSrc : in std_logic_vector(1 downto 0);
    wd     : in std_logic_vector(31 downto 0);
    op     : out std_logic_vector(6 downto 0);
    funct3 : out std_logic_vector(2 downto 0);
    funct7 : out std_logic_vector(6 downto 0);
    rd1    : out std_logic_vector(31 downto 0);
    rd2    : out std_logic_vector(31 downto 0);
    immExt : out std_logic_vector(31 downto 0);
  );
end idecoder;
```

-- instruction
-- control signal (regwrite)
-- control signal (immSrcs)
-- write data
-- opcode
-- funct3
-- funct7
-- Read data 1
-- Read data 2
-- Immediate extend

